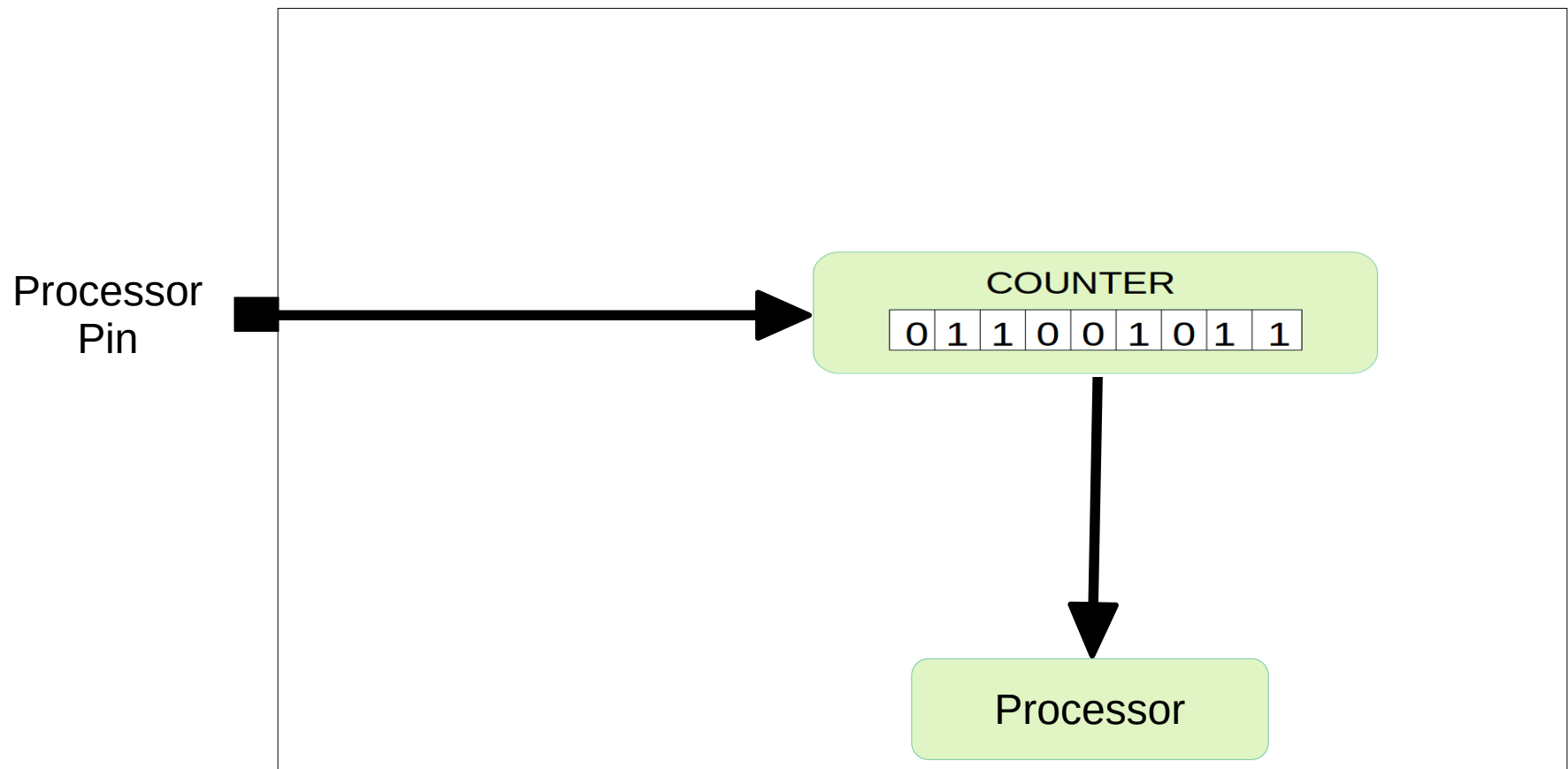


Timers and Counters

Ahmet Onat, 2022


Structure of a counter

- A pulse on an external pin increments or decrements the counter.
- Counter is a physical logic circuit. **It can count fast.**




Structure of a counter

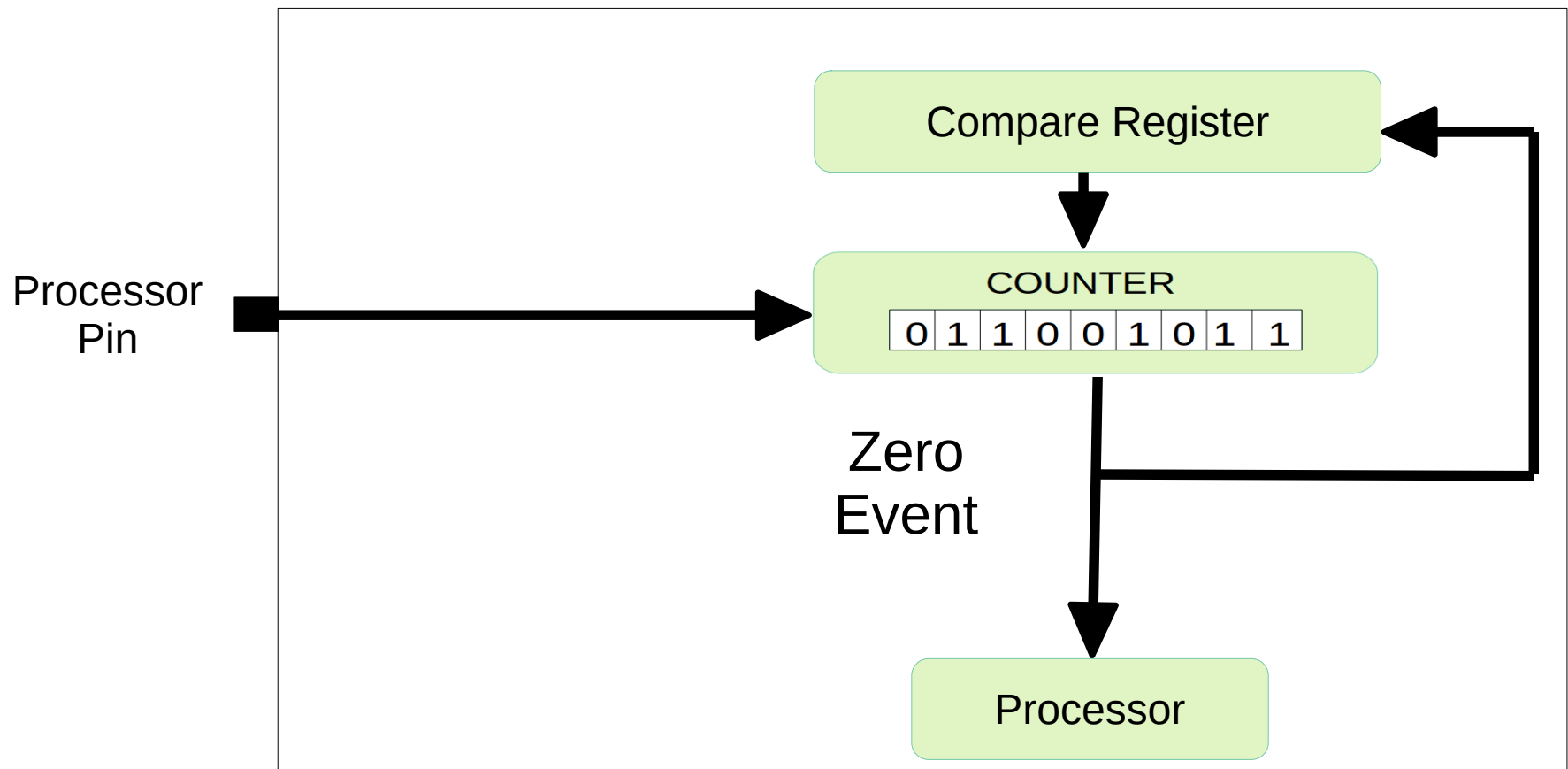- If the counter value equals Compare Register: Its value is re-set to zero.
- It can count groups of pulses.




Structure of a timer

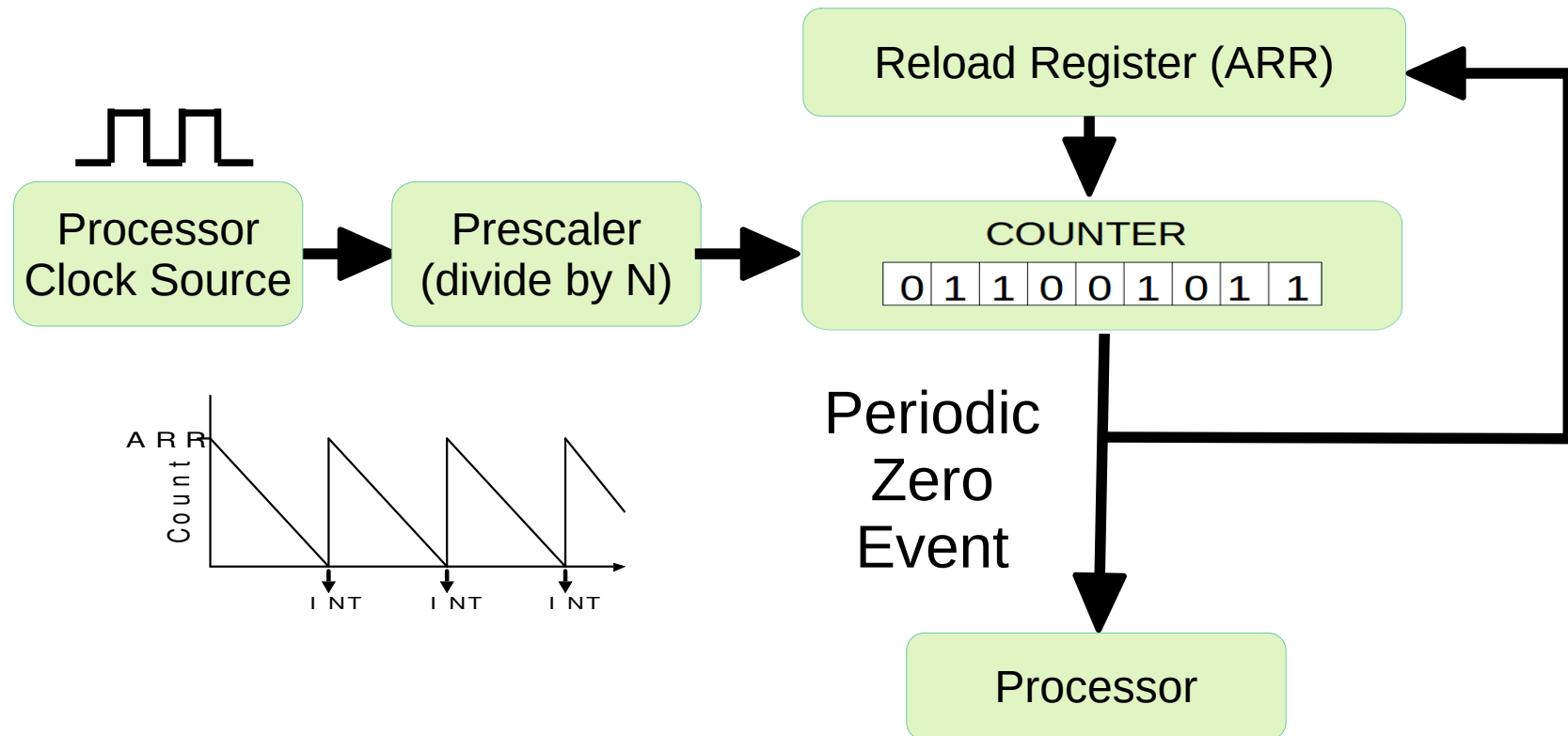- Same structure.
- But pulses are now provided by the processor clock.
- It now **functions as a timer**.




Structure of a timer

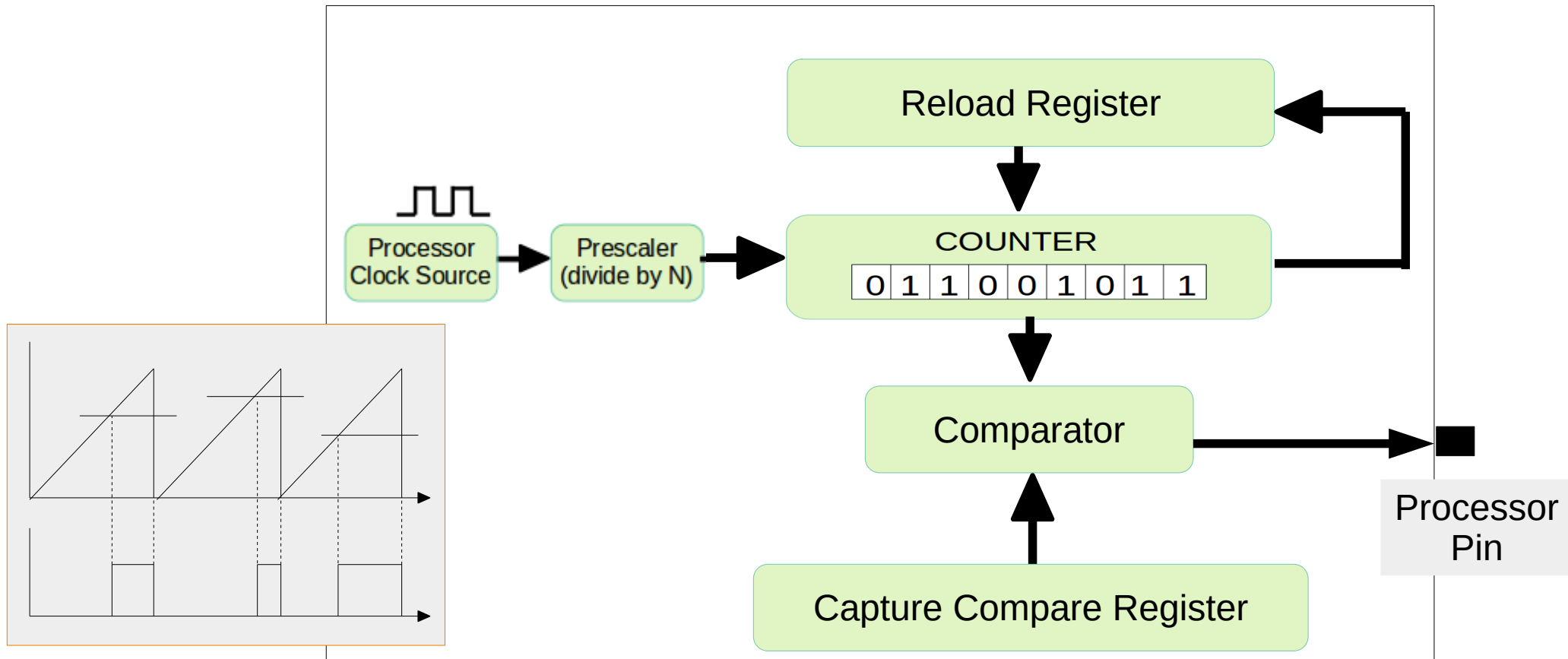- **Mode:** PWM generator
 - Value of reload register determines PWM frequency
 - Value of compare register determines duty cycle




Where timer-counters are used

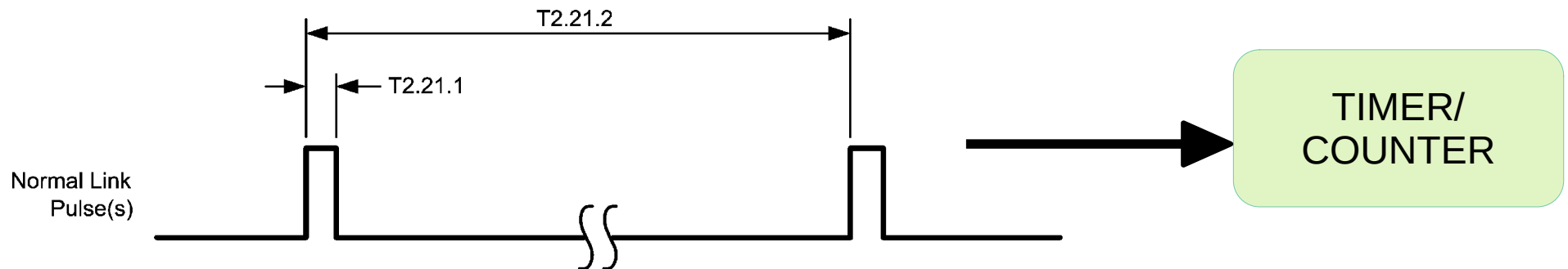- Timers are used to:
 - Time external events



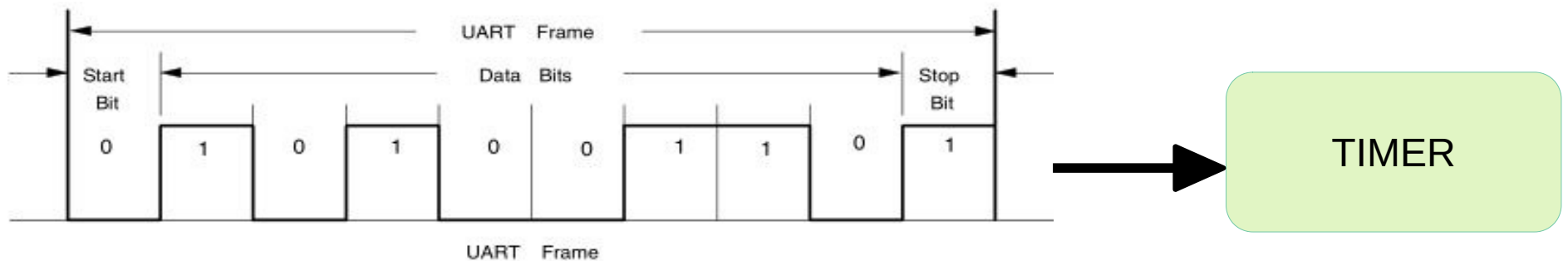
- Time '0' and '1' for incoming data stream (Ethernet, CAN...)




Network Data

Where timer-counters are used

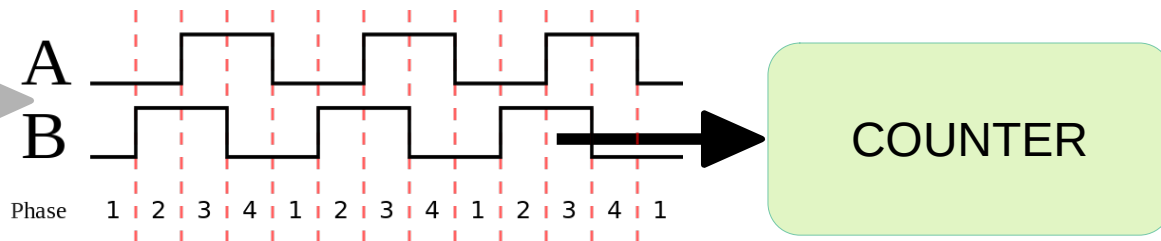- Timers are used to:
 - Count events (position encoder etc.)




- PWM generation (motor control etc.)

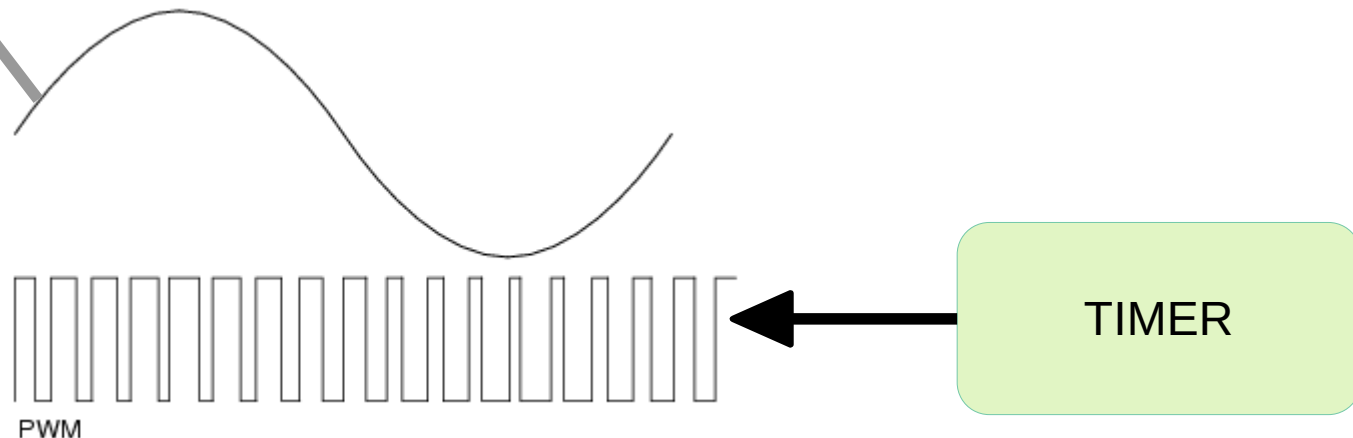


Where timer-counters are used

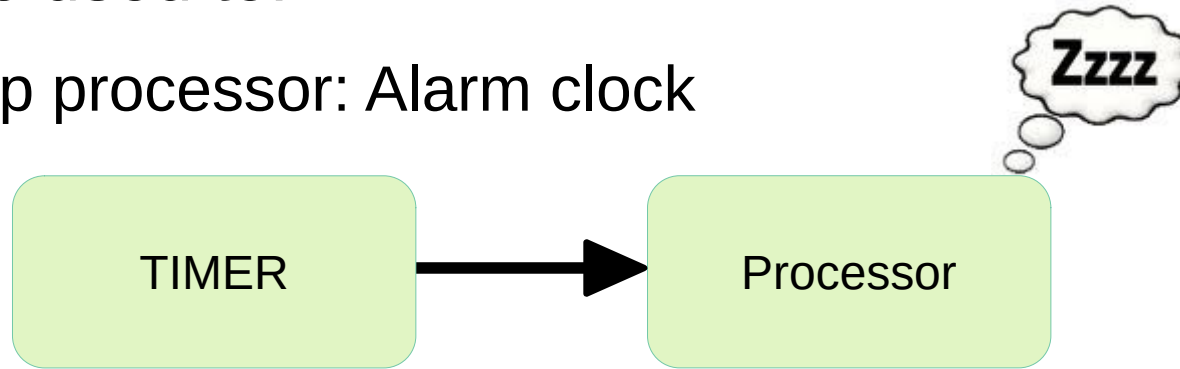- Timers are used to:
 - Wake up processor: Alarm clock



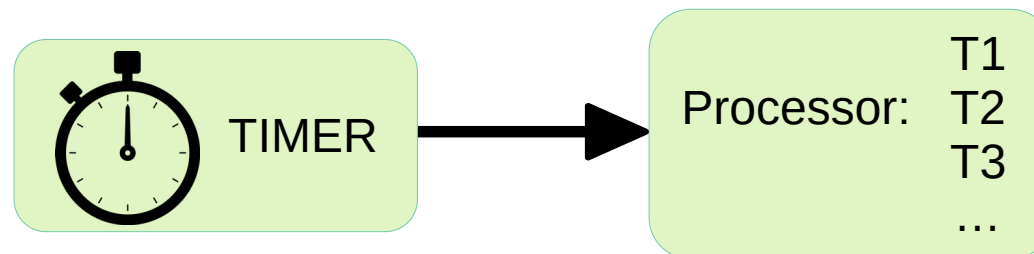
- OS: Generate periodic events to run periodic tasks.





Where timer-counters are used

- Timers are used to:

- Sampling

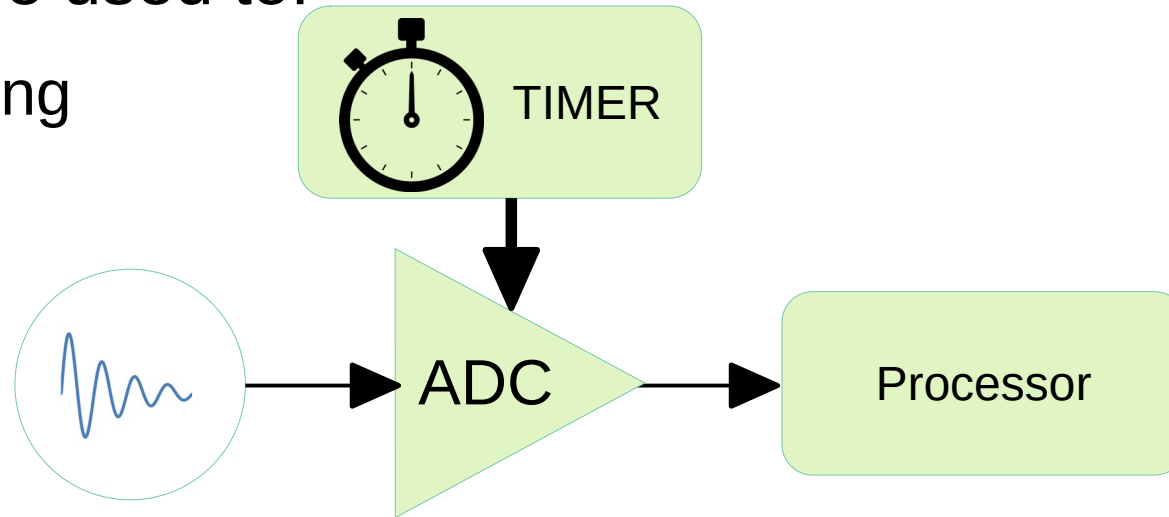


- Produce pulses

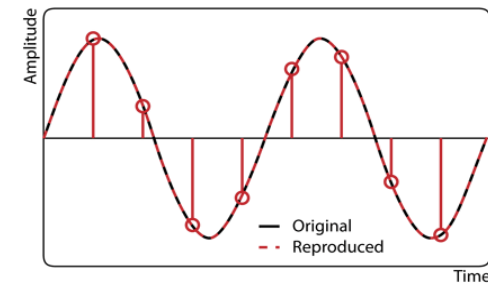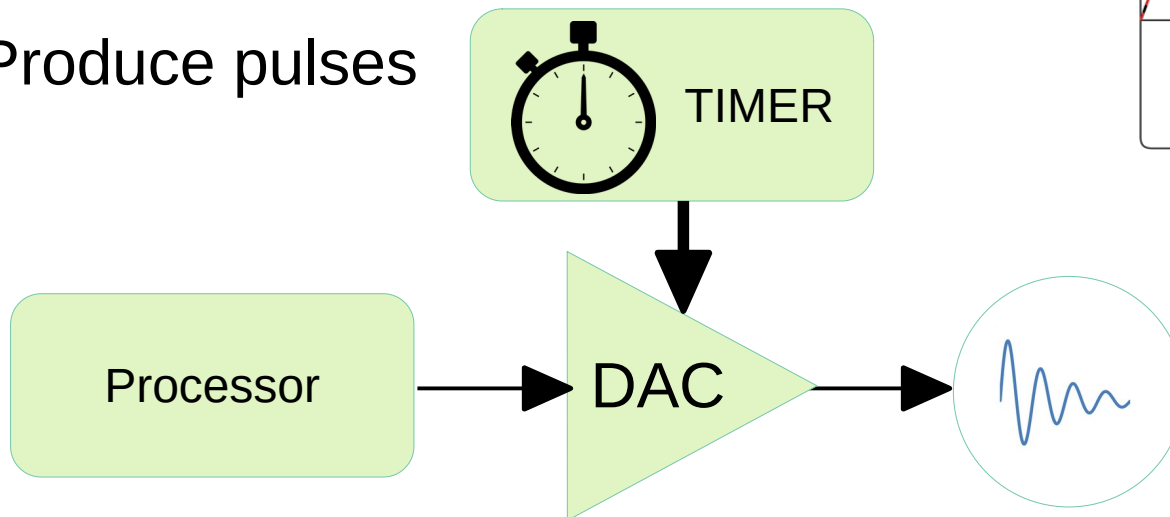


Where timer-counters are used

- **Mode:** Count external events

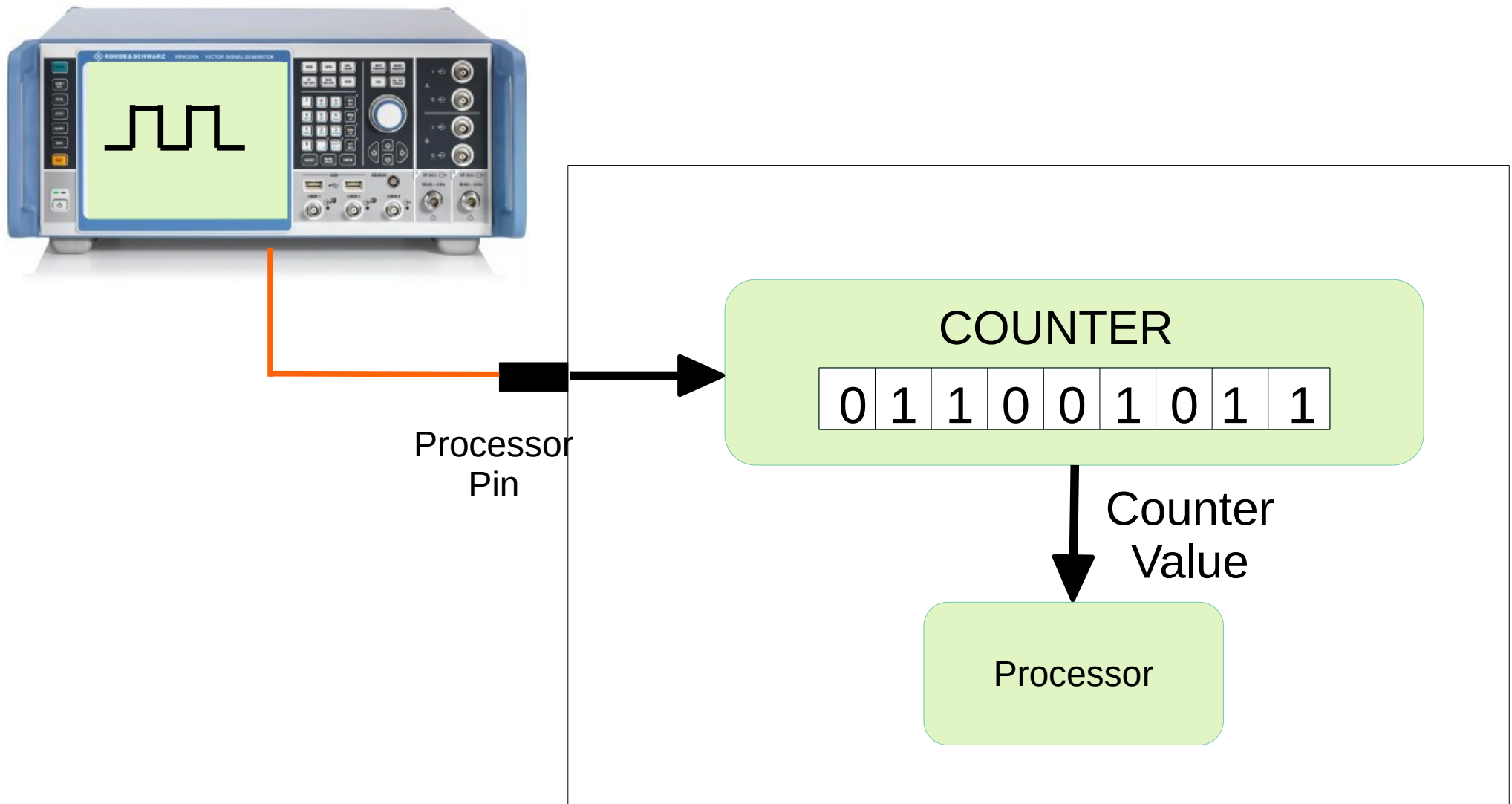

LPC824 SCT Block diagram

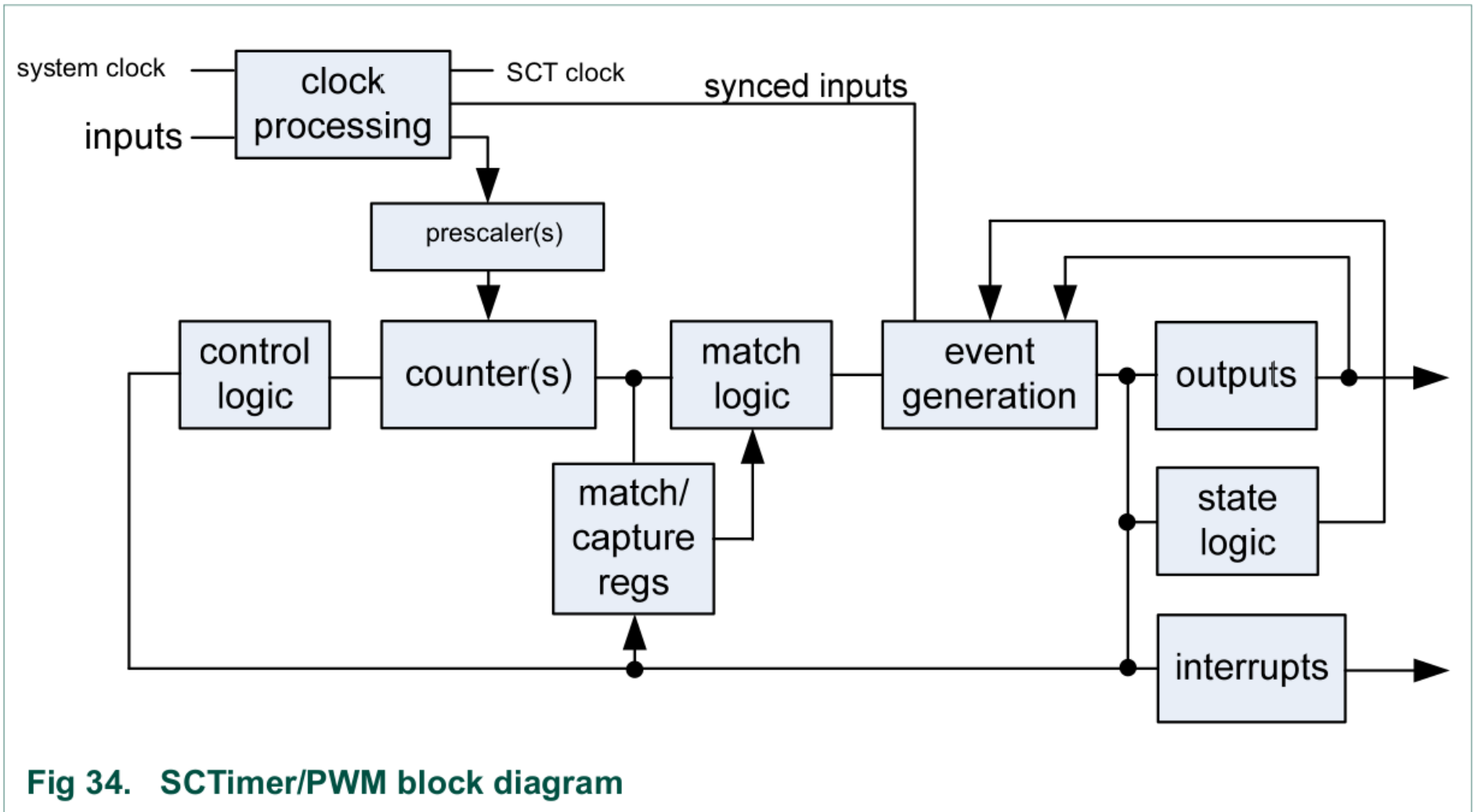

Source: NXP LPC824 User Manual Sec: 16.5 General description